

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

Integer Clock Divider



Motivation

From its name, an integer clock divider is a digital circuit that divides the frequency of a clock by an integer number.

For example, if I have a digital system that contains a CPU and a UART module, it is known that the CPU operates at a higher frequency than the UART. So, if the frequency of the system clock must be divided to a suitable value that the UART can operate at.

Another aspect that should be considered is power consumption. Dynamic power depends on the frequency of the clock signal, $P_{clk} = \frac{1}{2} \alpha C_L V_{DD}^2 f$, and if there are digital blocks with low performance, then we should divide its clock to reduce the power consumption.


There are two types of clock divider which are: synchronous and asynchronous. These types have opposite advantages and disadvantages which are summarized in the table below.
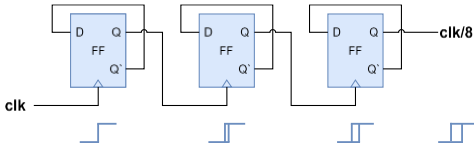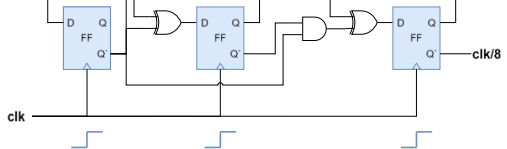
| | Asynchronous CLK Divider | Synchronous CLK Divider |
|---------------|--|---|
| Advantages | <ul style="list-style-type: none"> Each FF stage runs at lower clock frequency and hence reduces power consumption. Reduced loading on high frequency clock. | <ul style="list-style-type: none"> Reduced clock jitter |
| Disadvantages | <ul style="list-style-type: none"> Clock jitter accumulation | <ul style="list-style-type: none"> Each FF stage runs at higher clock frequency and hence increases power consumption. Large loading on high frequency clock. |
| Example |  |  |


Asynchronous Clock Divider

Clock Divider by 8

Block Diagram

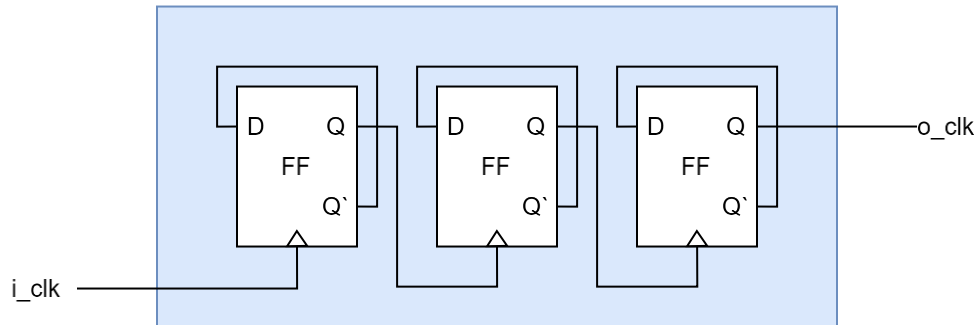

Waveform

 


RTL

[GitHub](#)

TB

[GitHub](#)


Simulation

 

Synchronous Clock Divider

Using Mod-N Counter: Clock Divider by 3


State Diagram

 


State Table

| Current State | | Next State | | | |
|---------------|----|------------|----|----|----|
| Q1 | Q0 | Q1 | Q0 | D1 | D0 |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |

Block Diagram

 

Waveform

 


RTL

[GitHub](#)

TB


[GitHub](#)

Simulation

 


Using T-FF: Odd Clock Divider

Block Diagram

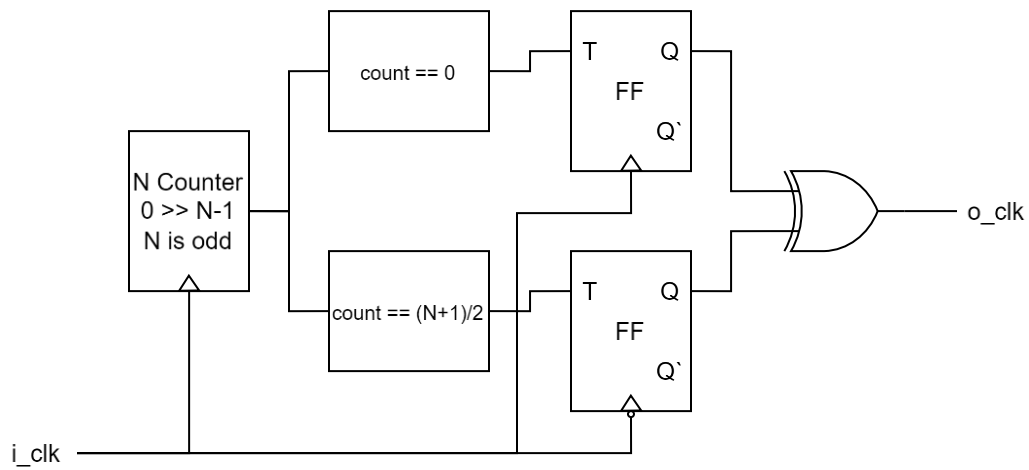

Waveform

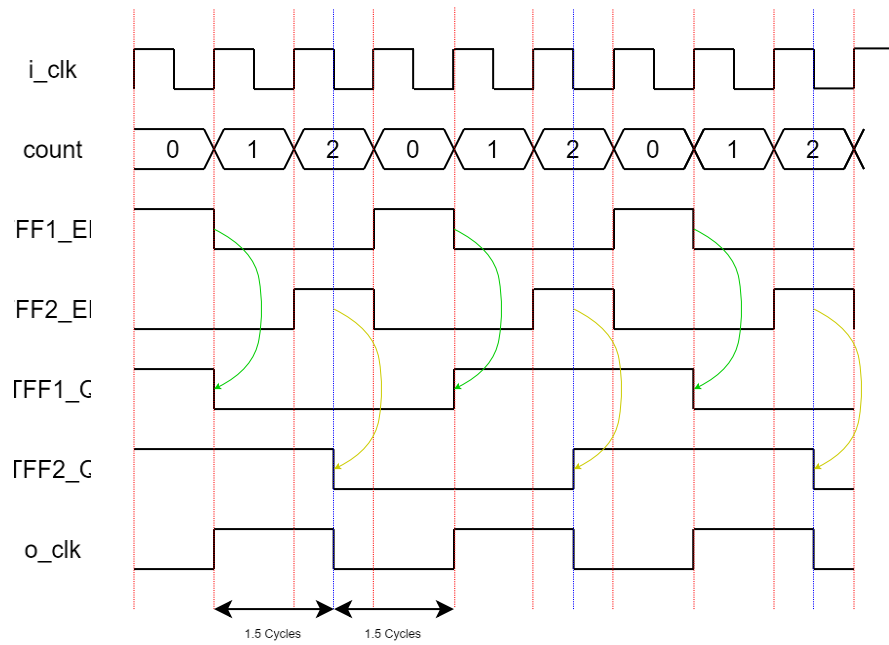


RTL

[GitHub](#)

TB


[GitHub](#)

Simulation

 


Using Ring Counter: Odd Clock Divider

Block Diagram

 

Waveform

 


RTL

[GitHub](#)

TB

[GitHub](#)

Simulation

 

Behavioral: Even Clock Divider

Idea

We use a counter to count to half the value of the divide ratio then we reset this counter.


RTL

[GitHub](#)

TB

[GitHub](#)

Simulation

 

General Clock Divider

Idea

We use two counters; one counts with positive edge of the clock and the other counts with negative edge of the clock and each one counts to the division ration – 1.

If the value of the counter is greater than division ratio divided by two, a pulse is generated.

Then to generate the divided clock, we OR the pulse signals generated from the two counters if the division ratio is odd number and if it is an even number, then the divided clock is the same as the pulse generated from the positive edge counter.

RTL


[GitHub](#)

TB

[GitHub](#)

Simulation

Even Ratio = 4

 

Odd Ratio = 7

